



COLLÈGE
DE FRANCE
1530



Chaire de Physique Mésoscopique
Michel Devoret
Année 2008, 13 mai - 24 juin

CIRCUITS ET SIGNAUX QUANTIQUES

QUANTUM SIGNALS AND CIRCUITS

Sixième Leçon / *Sixth Lecture*

This College de France document is for consultation only. Reproduction rights are reserved.

08-VI-1

VISIT THE WEBSITE OF THE CHAIR OF MESOSCOPIC PHYSICS

<http://www.college-de-france.fr>

then follow:

Enseignement > Sciences Physiques > Physique Mésoscopique > Site web

[PDF FILES OF LECTURES AND SEMINARS ARE POSTED
ON THIS WEBSITE](#)

Questions, comments and corrections are welcome!

write to "phymeso@gmail.com"

08-VI-2

CALENDAR OF SEMINARS

May 13: Denis Vion, (Quantronics group, SPEC-CEA Saclay)

Continuous dispersive quantum measurement of an electrical circuit

May 20: Bertrand Reulet (LPS Orsay)

Current fluctuations : beyond noise

June 3: Gilles Montambaux (LPS Orsay)

Quantum interferences in disordered systems

June 10: Patrice Roche (SPEC-CEA Saclay)

Determination of the coherence length in the Integer Quantum Hall regime

June 17: Olivier Buisson, (CRTBT-Grenoble)

A quantum circuit with several energy levels

June 24: Jérôme Lesueur (ESPCI)

High Tc Josephson Nanojunctions: Physics and Applications

08-VI-3

PROGRAM OF THIS YEAR'S LECTURES

Lecture I: Introduction and overview

Lecture II: Modes of a circuit and propagation of signals

Lecture III: The "atoms" of signal

Lecture IV: Quantum fluctuations in transmission lines

Lecture V: Introduction to non-linear active circuits

Lecture VI: Amplifying quantum signals with dispersive circuits

08-VI-4

LECTURE VI : AMPLIFYING QUANTUM SIGNALS WITH DISPERSIVE CIRCUITS

OUTLINE

1. Main ideas introduced in last lecture, purpose of this lecture
2. Minimal symplectic circuits are maximally efficient
3. Characteristics of amplifiers
4. Scattering matrix of minimal 1-port and 2-port active circuits
5. Ring modulator implementation of 2-port circuit

08-VI-5


OUTLINE

1. Main ideas introduced in last lecture, purpose of this lecture
2. Minimal symplectic circuits are maximally efficient
3. Characteristics of amplifiers
4. Scattering matrix of minimal 1-port and 2-port active circuits
5. Ring modulator implementation of 2-port circuit

08-VI-5a

PASSIVE vs ACTIVE LINEAR, DISPERSIVE 1-PORT

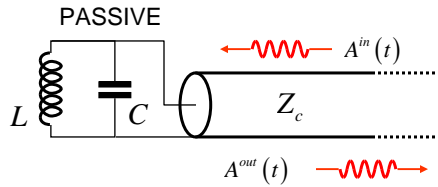Simplest example: LC. Both L and C are dispersive elements (no internal dissipation)




$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \Gamma = \frac{1}{2Z_c C}$$

generic frequency

$$\begin{bmatrix} a^{out}[\omega] \\ a^{out}[-\omega] \end{bmatrix} = \begin{bmatrix} r[\omega] & 0 \\ 0 & r[-\omega] \end{bmatrix} \begin{bmatrix} a^{in}[\omega] \\ a^{in}[-\omega] \end{bmatrix}$$

$$S^\dagger IS = I$$

UNITARY=
ORTHOGONAL
+ SYMPLECTIC

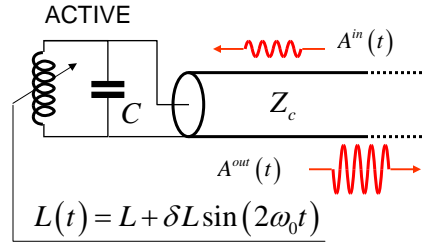

have treated only res. frequency case

$$\begin{bmatrix} a^{out}[\omega_0] \\ a^{out}[-\omega_0] \end{bmatrix} = \begin{bmatrix} r_0 & s_0 \\ s_0^* & r_0^* \end{bmatrix} \begin{bmatrix} a^{in}[\omega_0] \\ a^{in}[-\omega_0] \end{bmatrix}$$

$${}^t SJS = J$$

ONLY SYMPLECTIC

GENERALIZED S MATRIX

ENERGY NOT CONSERVED: POWER GAIN



08-VI-6c

PASSIVE S IN ROTATING WAVE APPROXIMATION

When $\frac{\Gamma}{\omega_0} = \kappa = \frac{1}{2Q} \ll 1$ we can consider only 1 pole affects the signal


$$r[\omega] = e^{i2\theta[\omega]} = -\frac{\omega_0^2 - \omega^2 - 2i\omega\Gamma}{\omega_0^2 - \omega^2 + 2i\omega\Gamma} \simeq \frac{1-i\frac{\omega - sgn(\omega)\omega_0}{\Gamma}}{1+i\frac{\omega - sgn(\omega)\omega_0}{\Gamma}}$$
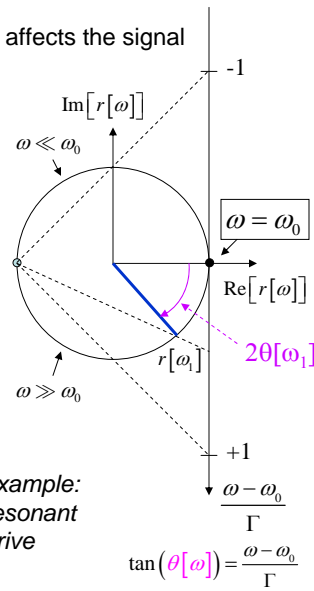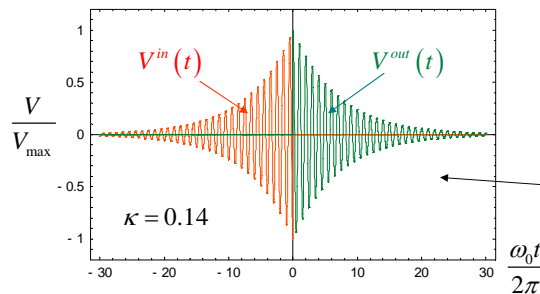
$$V[\omega] = (1+r[\omega])V^{in}[\omega] \simeq \frac{2}{1+i\frac{\omega - sgn(\omega)\omega_0}{\Gamma}} V^{in}[\omega]$$




08-VI-7b

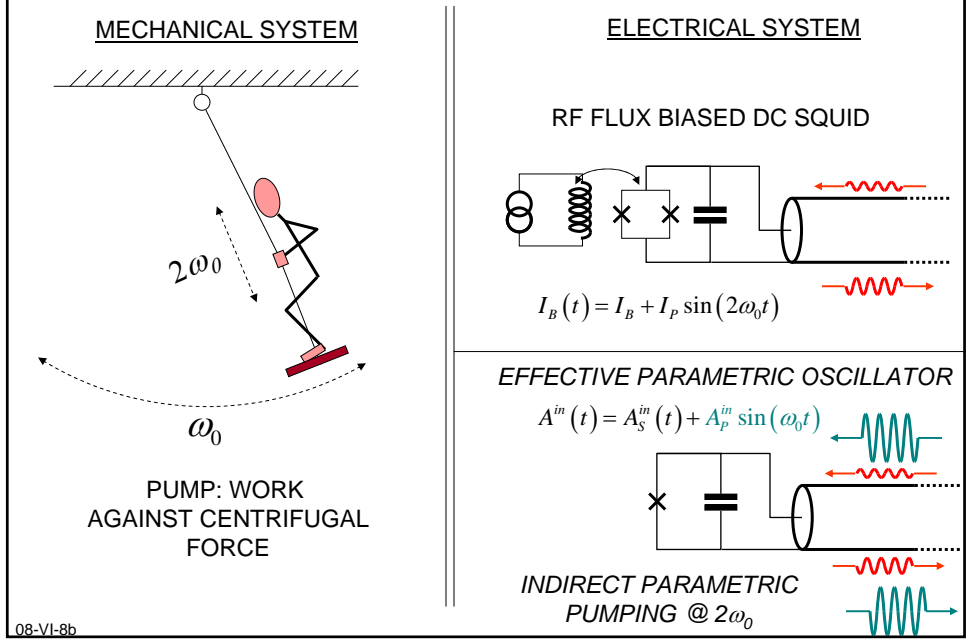EXAMPLES OF PARAMETRICALLY PUMPED OSCILLATORS



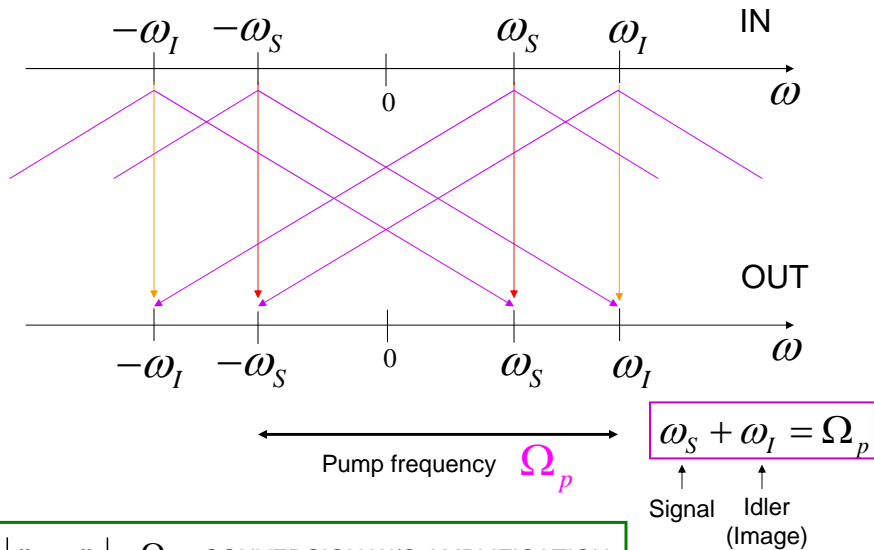IN NON-LINEAR ACTIVE DEVICE, SIGNALS SCATTER BETWEEN DIFFERENT FREQUENCIES



IF $|\omega_S - \omega_I| = \Omega_p$ CONVERSION W/O AMPLIFICATION

08-VI-9a

**PURPOSE OF THIS LECTURE:
EXPLAIN HOW MINIMAL, ACTIVE DISPERSIVE
CIRCUITS
PERFORM AMPLIFICATION AT QUANTUM LIMIT**

TWO MAIN ISSUES:

GAIN-BANDWIDTH TRADE-OFF

WHAT IS THE GENERALIZED SCATTERING MATRIX OF AN ACTIVE 1-PORT AND 2-PORT, BOTH AS A FUNCTION OF FREQUENCY OF SIGNALS AND AS A FUNCTION OF PUMP STRENGTH?

NOISE

HOW DO QUANTUM FLUCTUATIONS AFFECT THE NOISE OF THE AMPLIFIER?
WHAT IS THE MINIMAL AMOUNT OF NOISE ADDED BY THE AMPLIFIER?

IMPLEMENTATION ?

08-VI-10

OUTLINE

1. Main ideas introduced in last lecture, purpose of this lecture
2. Minimal symplectic circuits are maximally efficient
3. Characteristics of amplifiers
4. Scattering matrix of minimal 1-port and 2-port active circuits
5. Ring modulator implementation of 2-port circuit

08-VI-5b

GENERAL SCATTERING MATRIX

$$\vec{a}^{in} = \begin{bmatrix} a_1^{in} [+\omega_1] \\ a_1^{in} [-\omega_1] \\ a_2^{in} [+\omega_2] \\ a_2^{in} [-\omega_2] \\ \dots \\ a_i^{in} [+\omega_i] \\ a_i^{in} [-\omega_i] \end{bmatrix} \quad \vec{a}^{out} = \begin{bmatrix} a_1^{out} [+\omega_1] \\ a_1^{out} [-\omega_1] \\ a_2^{out} [+\omega_2] \\ a_2^{out} [-\omega_2] \\ \dots \\ a_i^{out} [+\omega_i] \\ a_i^{out} [-\omega_i] \end{bmatrix}$$

$$\vec{a}^{out} = \mathbf{S} \vec{a}^{in}$$

$$\sqrt{\frac{\hbar |\omega_l|}{2}} a_l [\omega_l] = A_l [\omega_l]$$

HERE,
WAVE AMPLITUDES
HAVE (PHOTON NB.)^{1/2}
DIMENSION
BUT ARE TREATED
CLASSICALLY

$$\mathbf{J} = \begin{bmatrix} 0 & 1 & 0 & 0 & \dots & \dots & 0 & 0 \\ -1 & 0 & 0 & 0 & \dots & \dots & 0 & 0 \\ 0 & 0 & 0 & 1 & \dots & \dots & 0 & 0 \\ 0 & 0 & -1 & 0 & \dots & \dots & 0 & 0 \\ \dots & \dots & \dots & \dots & \dots & \dots & \dots & \dots \\ \dots & \dots & \dots & \dots & \dots & \dots & \dots & \dots \\ 0 & 0 & 0 & 0 & \dots & \dots & 0 & 1 \\ 0 & 0 & 0 & 0 & \dots & \dots & -1 & 0 \end{bmatrix}$$

POISSON BRACKET:

$$\{u, v\}_{P.B.} = \mathbf{t} \left[\frac{\partial u}{\partial \vec{a}} \right] \mathbf{J} \left[\frac{\partial v}{\partial \vec{a}} \right]$$

see Goldstein, "Classical Mechanics" (Addison-Wesley 1980)

**S MATRIX MUST CONSERVE ALL
POISSON BRACKETS: S IS SYMPLECTIC**

$$\mathbf{t} \mathbf{S} \mathbf{J} \mathbf{S} = \mathbf{J}$$

SYMPLECTICITY CAN BE UNDERSTOOD AS INFORMATION CONSERVATION

08-VI-11b


TWO TYPES OF MAPS



ORTHOGONAL



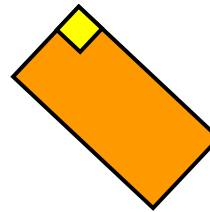CONSERVES
SYMMETRIC
BILINEAR FORM
(SCALAR PRODUCT)




lengths
and angles
preserved



SYMPLECTIC



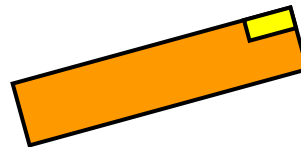CONSERVES
ANTISYMMETRIC
BILINEAR FORM
(EXTERIOR PRODUCT)



oriented areas
preserved

08-VI-12

SYMPLECTICITY IS A 1ST QUANTIZATION PROPERTY

HOWEVER

IT IS OFTEN EXPRESSED AS THE PROPERTY OF
CONSERVATION OF COMMUTATORS ...

$$\begin{aligned} \hat{X} &= \vec{x} \cdot \vec{\hat{a}} \\ \hat{Y} &= \vec{y} \cdot \vec{\hat{a}} \end{aligned} \quad \longrightarrow \quad [\hat{X}, \hat{Y}] = \vec{x} \cdot \mathbf{J} \cdot \vec{y} [\vec{\hat{a}}, \vec{\hat{a}}]$$

$$[\hat{X}^{out}, \hat{Y}^{out}] = [\hat{X}^{in}, \hat{Y}^{in}] \quad \longrightarrow \quad {}^t\text{SJS} = \mathbf{J}$$



... WHICH CAN BE MISLEADING!

08-VI-13

A MAXIMALLY EFFICIENT
SIGNAL PROCESSING FUNCTION
MIX THE MINIMAL NUMBER OF MODES
COMPATIBLE WITH SYMPLECTICITY

AMPLIFICATION: 2 CASES

08-VI-14a

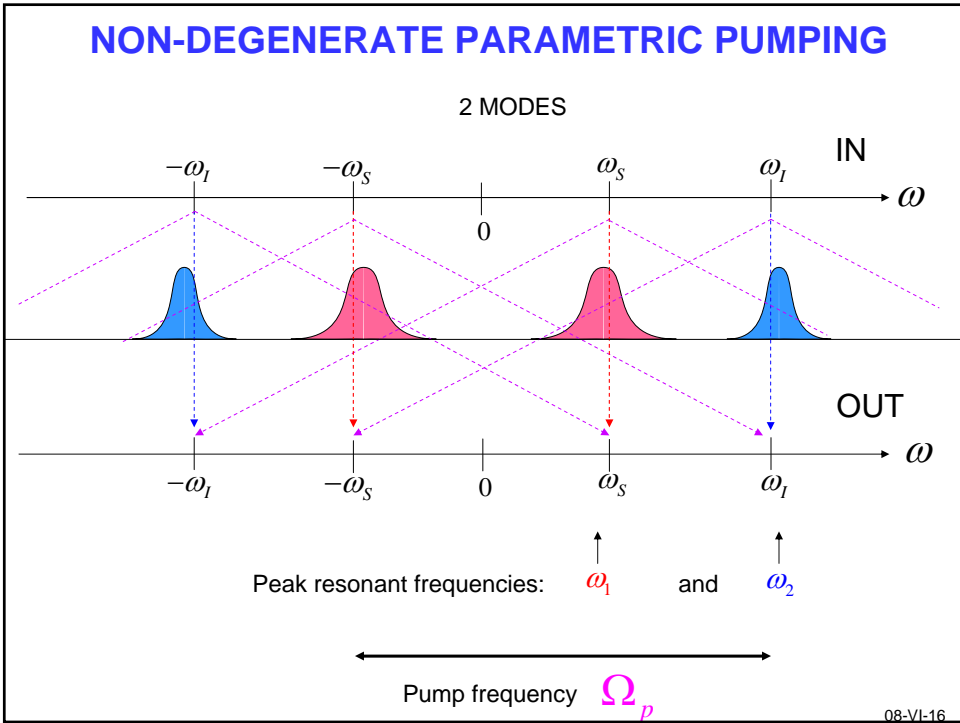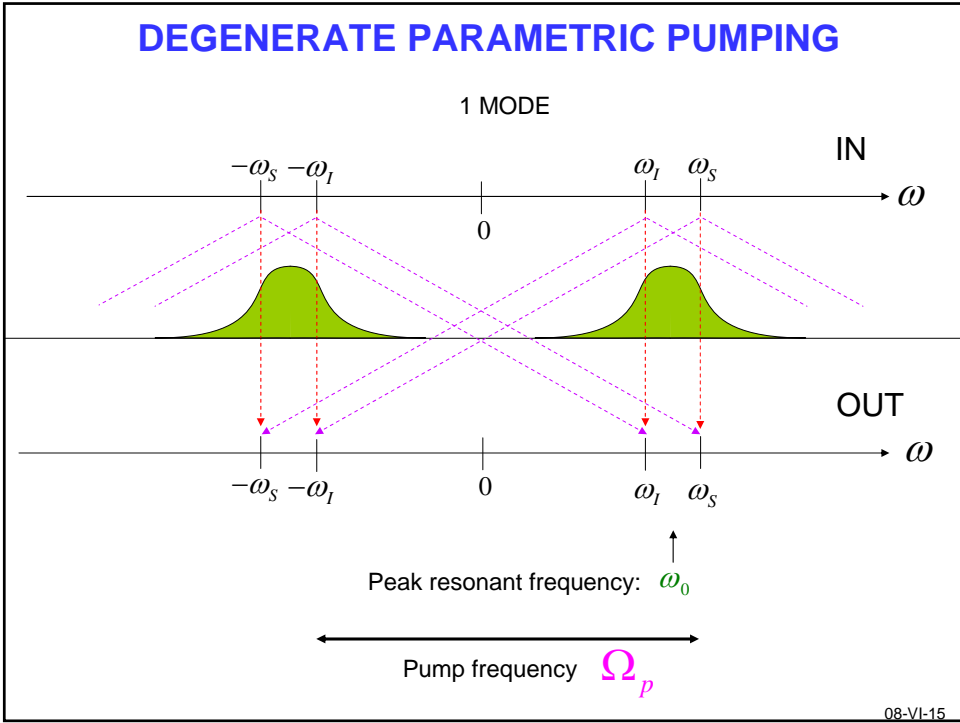


OUTLINE

1. Main ideas introduced in last lecture, purpose of this lecture
2. Minimal symplectic circuits are maximally efficient
3. Characteristics of amplifiers
4. Scattering matrix of minimal 1-port and 2-port active circuits
5. Ring modulator implementation of 2-port circuit

08-VI-5c

LINEAR AMPLIFIER CHARACTERISTICS

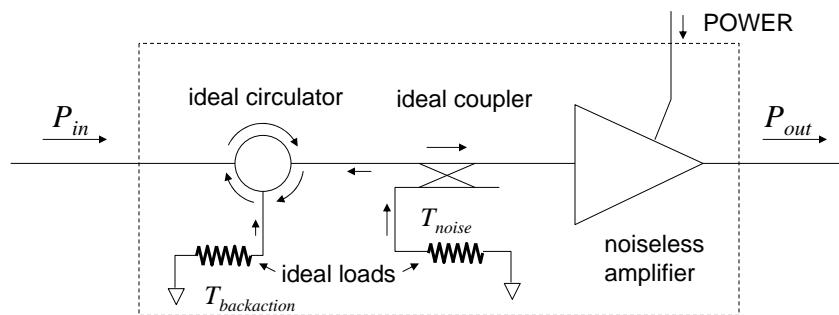


REPRESENTATION OF MATCHED 2-PORT


- Power gain (P_{out}/P_{in})
- Signal bandwidth
- Noise temperature T_{noise}
- Backaction $T_{backaction}$
- Dynamic range, intermodulation
- Tuning bandwidth

08-VI-17

2-PORT vs 1-PORT AMPLIFIER

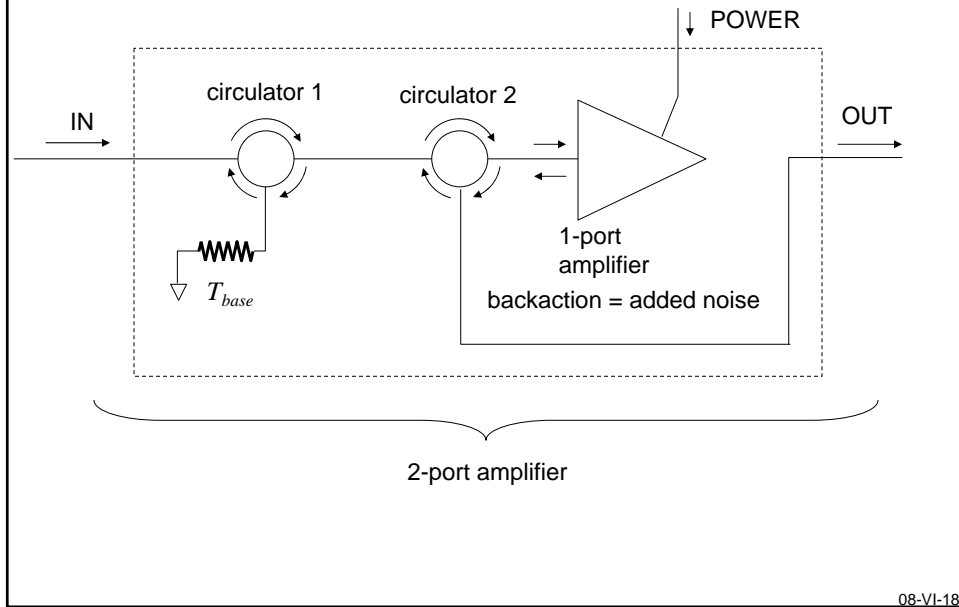

TWO TYPES OF LINEAR AMPLIFIERS

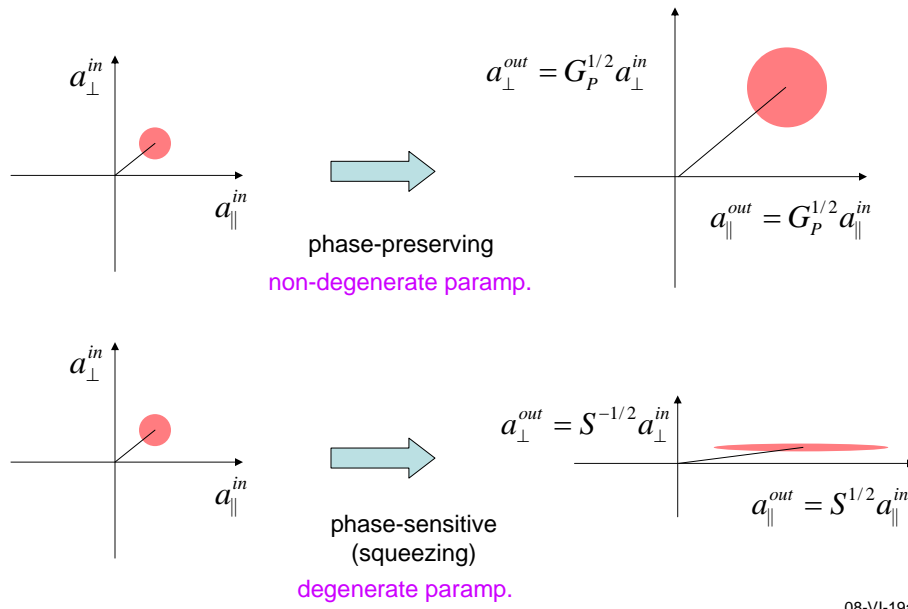

CRYOELECTRONIC AMPLIFIERS APPROACHING THE QUANTUM LIMIT

| <u>type</u> | $kT_N/(\hbar\omega/2)$ | <u>power gain</u> | <u>out-of-band back-action noise</u> | <u>ease of use</u> |
|-------------|------------------------|-------------------|--------------------------------------|--------------------|
| HEMT | 40-80 | 25-35dB | small | easy |
| SQUID | 1-2 | 20-30dB | concern | OK |
| RF-SET | 1-2 | 15-20 dB | concern | OK |
| QPC | 1 | ~0dB | very small | difficult |

HEMT: High Electron Mobility Transistor, SET: Single Electron Transistor, QPC: Quantum Point Contact

08-VI-20

LARGE GAIN LIMITS

PHASE-PRESERVING:

$$k_B T_N \geq \frac{\hbar \omega_s}{2}$$

STANDARD QUANTUM LIMIT

(Caves, 1982)

PHASE-SENSITIVE:

$$k_B T_N \geq 0$$

NOISELESS


08-VI-21

OUTLINE

1. Main ideas introduced in last lecture, purpose of this lecture
2. Minimal symplectic circuits are maximally efficient
3. Characteristics of amplifiers
4. Scattering matrix of minimal 1-port and 2-port active circuits
5. Ring modulator implementation of 2-port circuit

08-VI-5d

SCATTERING MATRIX OF DPA FOR ARBITRARY ω

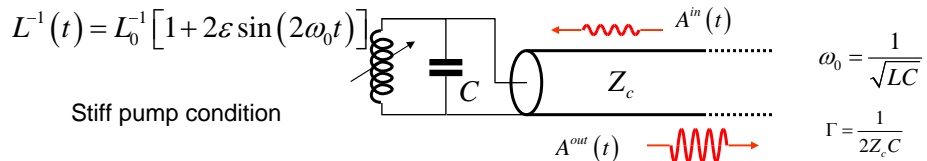

$$\ddot{\Phi} + 2\Gamma \dot{\Phi} + \omega_0^2 \Phi - i\omega_0^2 \varepsilon \Phi (e^{2i\omega_0 t} - e^{-2i\omega_0 t}) = 4\Gamma V^{in}(t) \quad V^{out}(t) = \dot{\Phi} - V^{in}(t)$$

Harmonic balance + RWA $\Rightarrow i\omega_0 \left[\frac{(\omega_0 - \omega)}{i\Gamma} - 1 \right] \Phi[\omega] - i \frac{\omega_0^2 \varepsilon}{2\Gamma} \Phi[\omega - 2\omega_0] = 2V^{in}[\omega]$

After a few steps:

$$\begin{bmatrix} A^{out} [+\omega_s] \\ A^{out} [-\omega_s] \\ A^{out} [+\omega_l] \\ A^{out} [-\omega_l] \end{bmatrix} = \begin{bmatrix} r & 0 & 0 & s \\ 0 & r^* & s^* & 0 \\ 0 & s^* & r^* & 0 \\ s & 0 & 0 & r \end{bmatrix} \begin{bmatrix} A^{in} [+\omega_s] \\ A^{in} [-\omega_s] \\ A^{in} [+\omega_l] \\ A^{in} [-\omega_l] \end{bmatrix}$$

$$r = \frac{1 + \mathcal{G}^2 + \zeta^2}{(1 - i\mathcal{G})^2 - \zeta^2}$$


$$s = \frac{2\zeta}{(1 - i\mathcal{G})^2 - \zeta^2}$$

$$\zeta = \varepsilon \frac{\omega_0}{2\Gamma} < 1$$

SYMPLECTICITY: $\begin{cases} |r|^2 - |s|^2 = 1 \\ rs^* - r^*s = 0 \end{cases}$ $\mathcal{G} = \tan \theta = \frac{\omega_s - \omega_0}{\Gamma}$

08-VI-21d

GAIN-BANDWIDTH COMPROMISE

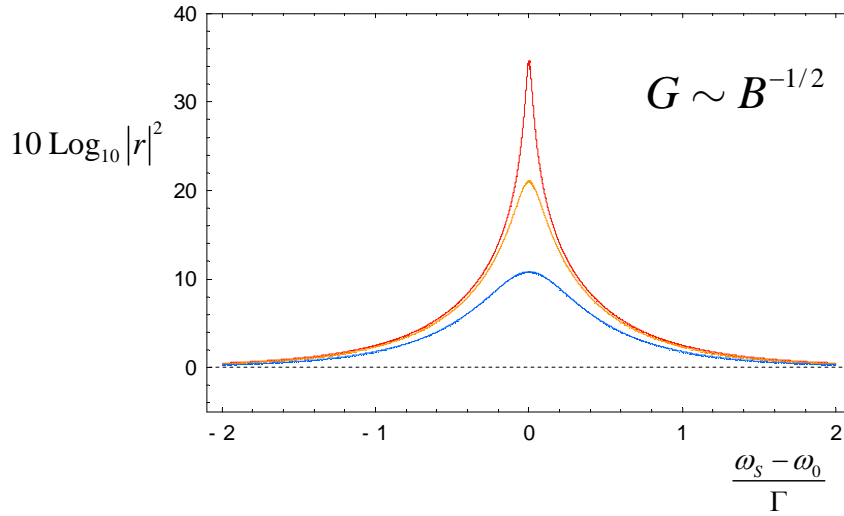



See experiment by MA Castellanos-Beltran & K. Lehnert, arXiv:0706.2373v

08-VI-22

MINIMAL IMPLEMENTATION OF NON-DEGENERATE PARAMETRIC AMPLIFIER

TIME-DEPENDENT
COUPLING BETWEEN
2 OSCILLATORS
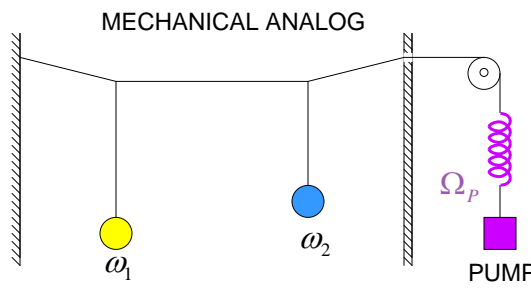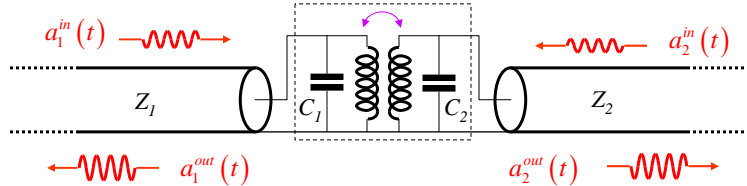
$$(L^{-1})_{12} = (L_0^{-1})_{12} [1 + 2\varepsilon \sin(\Omega_p t)]$$




HERE,
WAVE AMPLITUDES
HAVE (PHOTON NB.)^{1/2}
DIMENSION
BUT ARE TREATED
CLASSICALLY


$$\sqrt{\frac{\hbar|\omega_i|}{2}} a_i[\omega_i] = A_i[\omega_i]$$

08-VI-23

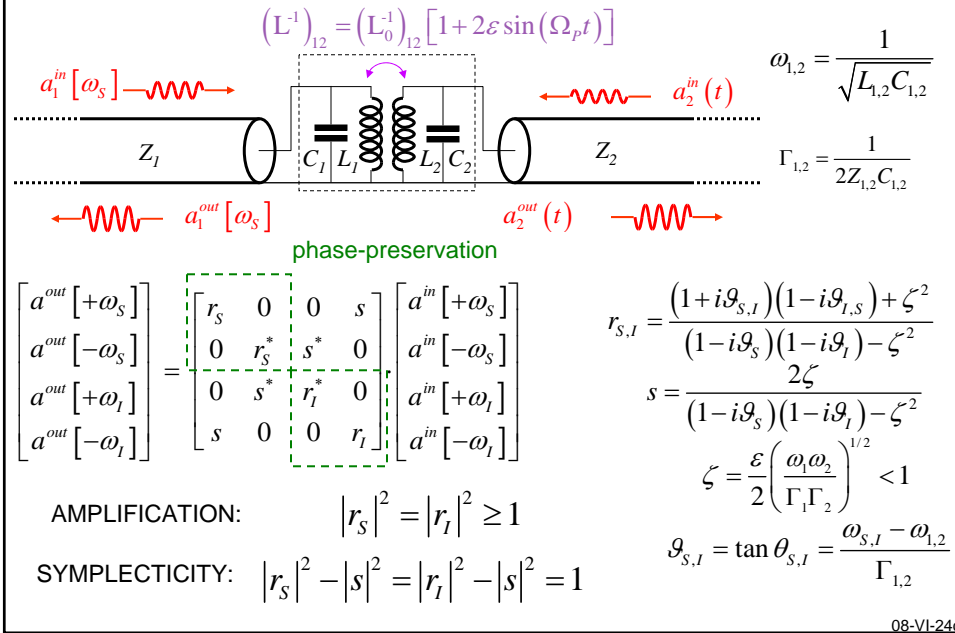
SCATTERING MATRIX OF NDPA FOR ARBITRARY ω



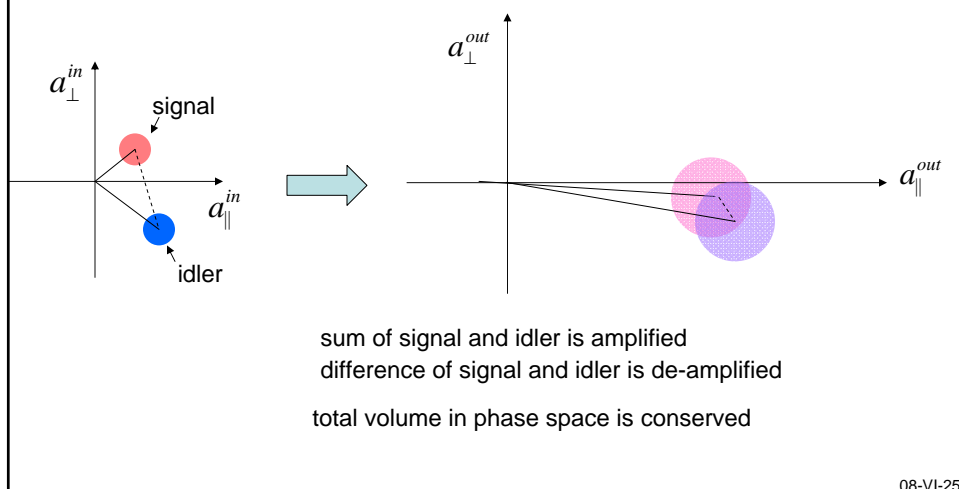SIGNAL AND IDLER CO-AMPLIFICATION FOR NON-DEGENERATE PARAMETRIC AMPLIFIER



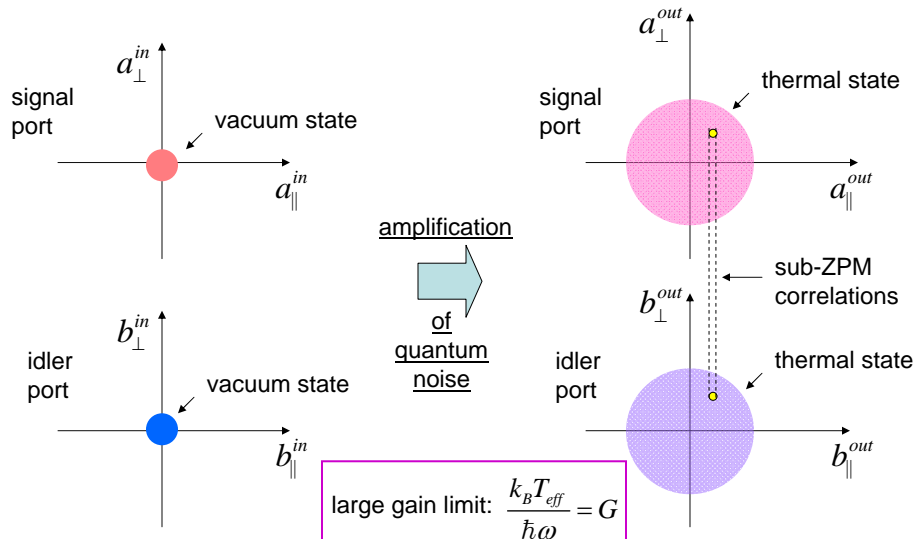SQUEEZING OF QUANTUM FLUCTUATIONS FOR FOR NON-DEGENERATE PARAMETRIC AMPLIFIER



see "Quantum Squeezing", Drummond and Ficek eds (Springer 2004)

08-VI-26d


OUTLINE

1. Main ideas introduced in last lecture, purpose of this lecture
2. Minimal symplectic circuits are maximally efficient
3. Characteristics of amplifiers
4. Scattering matrix of minimal 1-port and 2-port active circuits
5. Ring modulator implementation of 2-port circuit

08-VI-5e



TOWARDS THE PUREST NON-LINEARITY: THE JOSEPHSON RING MODULATOR

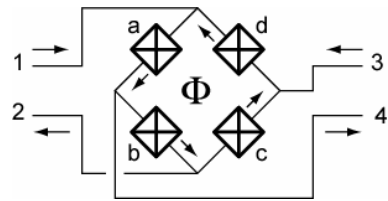(Bergeal *et al.*, 2008, arXiv:0805.3452)



4 junctions in a ring threaded by flux

4 modes:

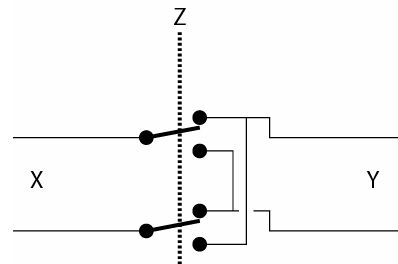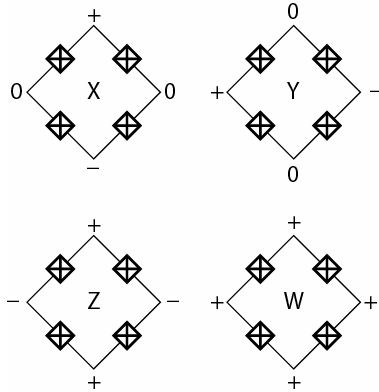

The Z mode can be understood as providing an invertible coupling between the X and Y mode


08-VI-27

CONSEQUENCES OF RING SYMMETRY

- Coexistence of 2 stable states with $4\Phi_0$ -periodicity

junction phases satisfy
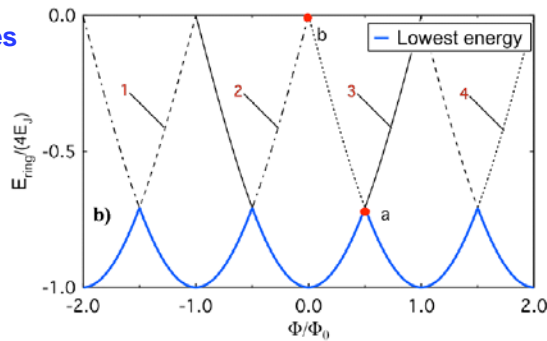
$$\begin{cases} \phi_a + \phi_b + \phi_c + \phi_d = \frac{2\pi\Phi}{\Phi_0} \\ \sin \phi_a = \sin \phi_b = \sin \phi_c = \sin \phi_d \end{cases}$$



- Useful non-linearity with minimal number of spurious terms

At $\Phi = \Phi_0/2$ and for small X, Y, Z :


$$E_{ring} = \underbrace{\Xi XYZ}_{\text{Mix 3 orthogonal modes X, Y, Z (S. Girvin)}} + B \underbrace{\left(\frac{X^2}{4} + \frac{Y^2}{4} + \frac{Z^2}{2} \right)}_{\text{Spurious terms only renormalize mode frequencies}} + \text{higher order terms}$$

Mix 3 orthogonal modes X, Y, Z (S. Girvin)


Spurious terms only renormalize mode frequencies

08-VI-28

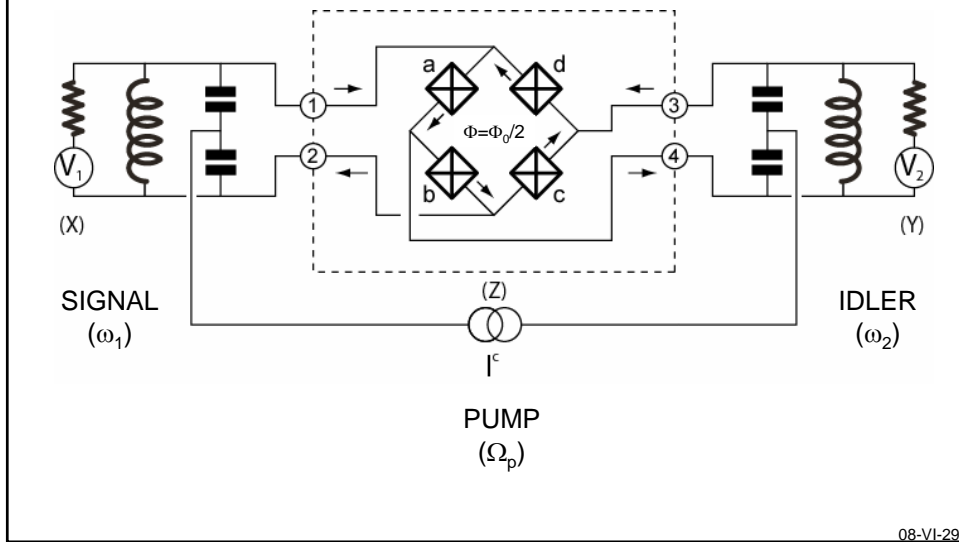SCHEMATICS OF JOSEPHSON AMPLIFIER BASED ON RING MODULATOR





JOSEPHSON PARAMETRIC AMPLIFIER CHIP

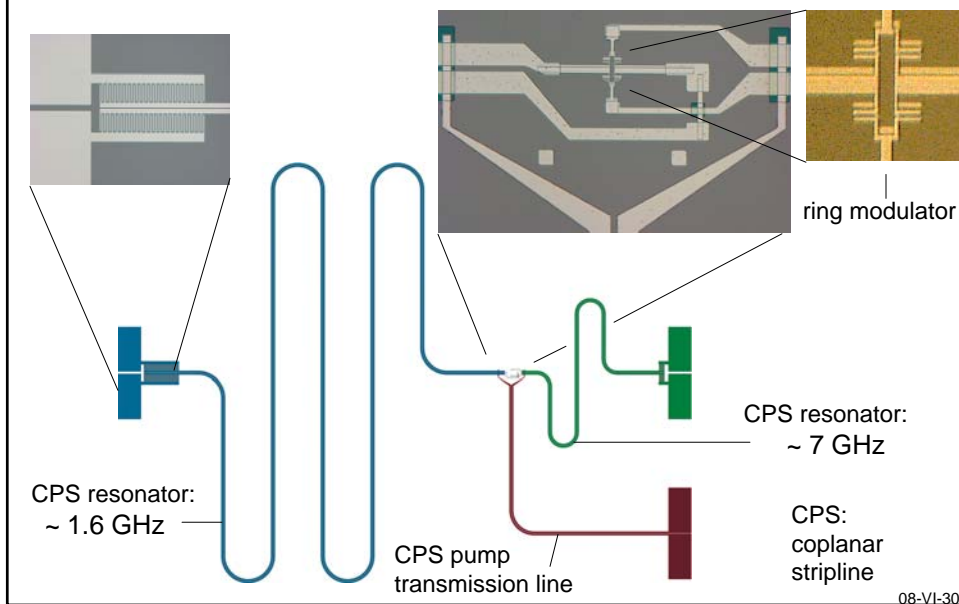


2-MODE NOISE SQUEEZING DATA

(Bergeal *et al.*, 2008)

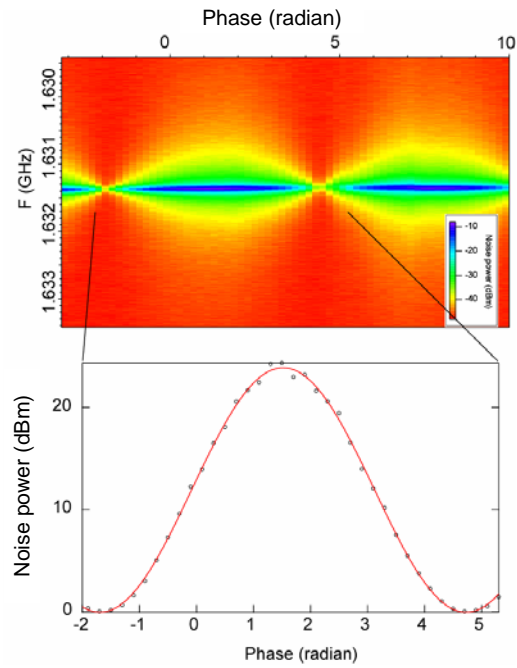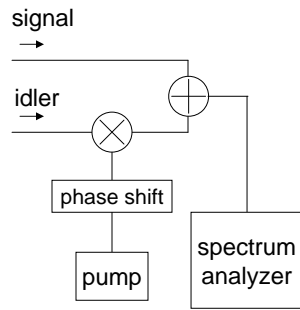

2-MODE NOISE SQUEEZING DATA (CTND)

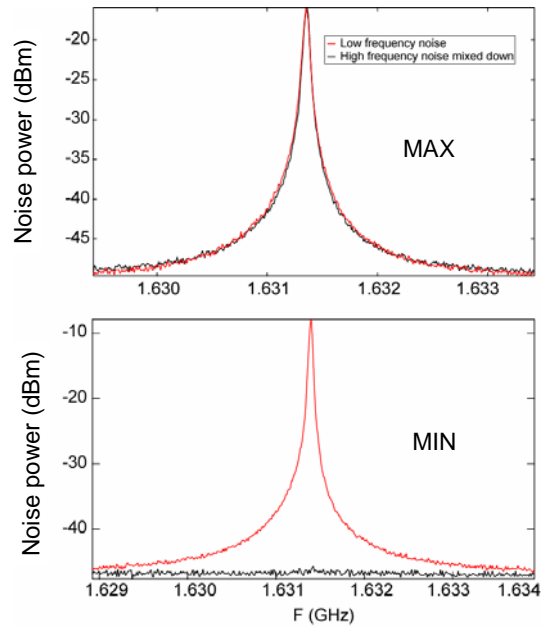

CONCLUSIONS

A PHASE PRESERVING AMPLIFIER ADDS AT LEAST HALF A PHOTON OF NOISE AT THE SIGNAL FREQUENCY

A PHASE SENSITIVE AMPLIFIER CAN BE NOISELESS

MINIMAL NUMBER OF MODES IN A DISPERSIVE ACTIVE CIRCUIT IS A NECESSARY CONDITION FOR AMPLIFICATION AT THE QUANTUM LIMIT

PARAMETRIC AMPLIFICATION USING 3-WAVE OR 4-WAVE MIXING OF JOSEPHSON JUNCTION IS MINIMAL

JOSEPHSON RING MODULATOR IS A CONVENIENT PURE 3-WAVE MIXING DEVICE FOR NON-DEGENERATE PARAMETRIC AMPLIFICATION

08-VI-30

NEXT YEAR :

1) NON-PERTURBATIVE ASPECTS OF QUANTUM CIRCUITS

2) PERIODICITY OF JOSEPHSON COSINE POTENTIAL AND ITS CONSEQUENCES

3) STRONG COUPLING BETWEEN JUNCTION AND REST OF CIRCUIT

4) STRONG DAMPING WITH NORMAL TUNNEL JUNCTIONS

08-VI-31

THANKS TO:

N. Bergeal, M. Brink, D. Esteve, L. Frunzio, S. Girvin, B. Huard, P. Joyez, A. Kamal, H. Pothier, D. Prober, F. Schackert, R. Schoelkopf, I. Siddiqi, C. Urbina, R. Vijay and D. Vion

RESEARCH SUPPORTED BY:



W.M.
KECK



COLLÈGE
DE FRANCE
—1530—



END OF 2008 LECTURES